

Circuit diagram

I2c lcd pins

Sda- ESP PIN D21

SCL – ESP PIN D22

MQ – 135 PINS

AO – ESP PIN VP

DHT 11

DATA- ESP PIN D4

POWER

ESP VIN-I2C VCC

ESP GND - I2C GND

ESP 3.3V - MQ-135, DHT 11 VCC PIN //SPLITE THE CABLE

ESP GND – MQ-135, DHT 11 GND PIN // SPLITE THE CABLE

IF YOU ARE HAVING PROBLEM TO SPLITE THE CABLE Comment
YOUR PROBLEM

IF YOU DON'T WANT TO BUILD YOU CAN ORDER CUSTOM MADE
PROBUCT FROM everythingcustom.netlify.app
